



## Design Example Report

<b>Title</b>	<b><i>8.75 W Power Supply using TNY268P</i></b>
<b>Specification</b>	Input: 90 – 265VAC Output: 3.5V / 2.5A (4A peak)
<b>Application</b>	Adapter
<b>Author</b>	Power Integrations Applications Department
<b>Document Number</b>	DER-60
<b>Date</b>	May 27, 2005
<b>Revision</b>	1.0

### Summary and Features

- Low cost, low parts count.
- No Y1 Safety capacitor to pass EN55022B.
- No load input power < 300mw @ 265VAC.
- Meet CEC requirement with 3.3V2.5A/ 1.8M 18AWG output cable.
- Meet LPS < 17.5W with full range input.
- OTP, OVP latch function.

The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at [www.powerint.com](http://www.powerint.com).

## Table Of Contents

1	Introduction.....	3
2	Power Supply Specification.....	4
3	Schematic.....	5
4	Circuit Description .....	6
4.1	Input Rectification and EMI Filtering.....	6
4.2	TOPSwitch Primary.....	6
4.3	Output Rectification.....	6
4.4	Output Feedback.....	6
4.5	OTP, OVP and LPS Protection Circuit .....	7
5	PCB Layout .....	8
6	Bill Of Materials .....	9
7	Transformer Specification.....	10
7.1	Electrical Diagram .....	10
7.2	Electrical Specifications.....	10
7.3	Materials.....	10
7.4	Transformer Build Diagram .....	11
7.5	Transformer Construction.....	11
8	Transformer Spreadsheets.....	12
9	Performance Data .....	15
9.1	Efficiency.....	15
9.2	No-load Input Power.....	16
9.3	Regulation .....	17
9.3.1	Load.....	17
9.3.2	Line .....	17
10	Waveforms.....	18
10.1	Drain Voltage and Current, Normal Operation .....	18
10.2	Output Voltage Start-up Profile .....	19
10.3	Max Output Power (LPS) Testing (Specification $P_o < 17.5w$ ) .....	19
10.4	Load Transient Response .....	20
10.5	Output Ripple Measurements.....	21
10.5.1	Ripple Measurement Technique .....	21
10.5.2	Measurement Results .....	22
11	Conducted EMI .....	23
12	Revision History.....	24

### Important Note:

Although this board is designed to satisfy safety isolation requirements, the engineering prototype has not been agency approved. Therefore, all testing should be performed using an isolation transformer to provide the AC input to the prototype board.


Design Reports contain a power supply design specification, schematic, bill of materials, and transformer documentation. Performance data and typical operation characteristics are included. Typically only a single prototype has been built.



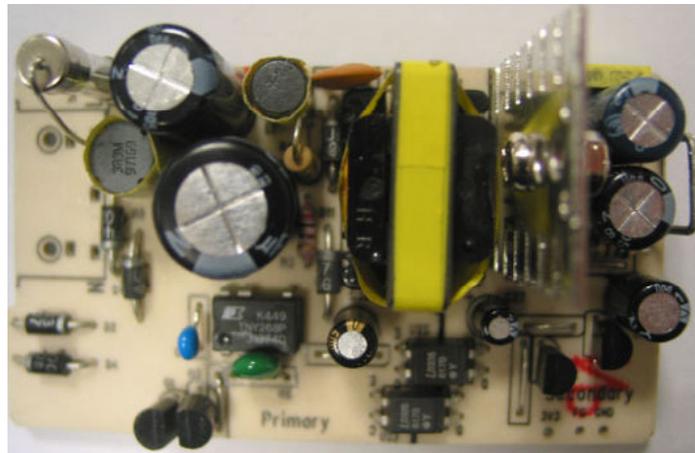
## 1 Introduction

This document is an engineering report describing an adapter power supply utilizing a TNY268P. This power supply is intended as a general purpose evaluation platform for TNY268P.

The document contains the power supply specification, schematic, bill of materials, transformer documentation, printed circuit layout, and performance data.



(Component side)

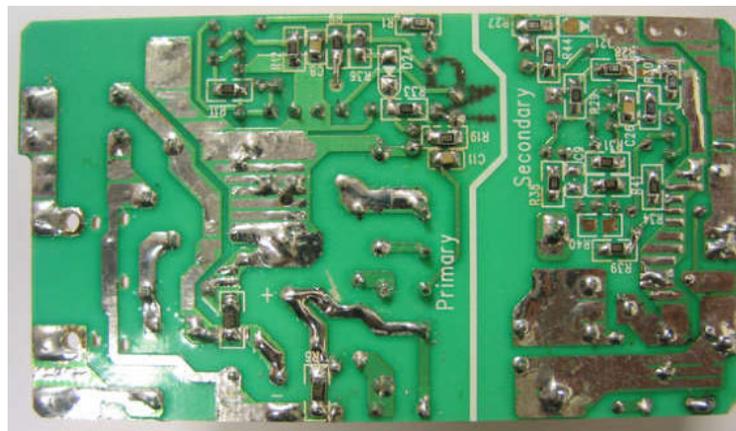

(Solder side)

**Figure 1** – Populated Circuit Board Photograph

## 2 Power Supply Specification

Description	Symbol	Min	Typ	Max	Units	Comment
<b>Input</b>						
Voltage	$V_{IN}$	85		265	VAC	2 Wire – no P.E.
Frequency	$f_{LINE}$	47	50/60	64	Hz	
No-load Input Power (240 VAC)				0.3	W	
<b>Output</b>						
Output Voltage 1	$V_{OUT1}$	3.3	3.5	3.7	V	± 5% 20 MHz bandwidth
Output Ripple Voltage 1	$V_{RIPPLE1}$		300	400	mV	
Output Current 1	$I_{OUT1}$			2.5	A	
<b>Total Output Power</b>						
Continuous Output Power	$P_{OUT}$			8.75	W	
Peak Output Power	$P_{OUT\_PEAK}$			14	W	
<b>Efficiency</b>	$\eta$		70		%	Measured at $P_{OUT}$ (8.75 W), 25 °C
<b>CEC Efficiency</b> (115VAC and 230VAC)	<b>Avg. <math>\eta</math></b>	68.6			%	Avg. Eff. At 25%, 50%, 75% and 100% load
<b>Environmental</b>						
Conducted EMI						Meets CISPR22B / EN55022B Designed to meet IEC950, UL1950 Class II
Safety						
Ambient Temperature	$T_{AMB}$	0		40	°C	Free convection, sea level





## 4 Circuit Description

A Flyback converter is used to obtain 3.5V 2.5A output from 90-265 VAC input. The bias winding, which also serves as core cancellation winding to reduce EMI noise, provides current to the BP pin of TNY268P, to reduce the No-Load Input Power consumption by about 0.1 W.

### 4.1 Input Rectification and EMI Filtering

Fuse F1 protects the charger against any fault condition, and input current exceeds 1A. Diodes D1, D2, D3, and D4 form Full-bridge rectifier, and rectify the AC voltage into DC voltage and charge the capacitors C1 and C2. L1, L2, C1, and C2 form  $\pi$  – filter and attenuate EMI noise. Here, C1 and C2 act as both storage capacitors and part of EMI filter, which reduces the total cost.

### 4.2 TOPSwitch Primary

This design uses RCD (C3, D5, R4, and R3) clamping across primary winding to limit the drain voltage below 700V, when the Mosfet inside U1 turns OFF. The capacitor C4 connected to BP (by-pass) pin of U1 stores energy and provide power for the internal circuit of U1 and also to turn ON the U1's Mosfet, during power-up and steady state operation. C11, D11, and R19 form bias supply components, which provide power to the BP pin during steady state operation. This will reduce the No-load input power consumption. R45 limits the current flowing to BP pin, and it is tuned to reduce the No-load input power to minimum. The opto-coupler transistor pulls down enable (EN) pin of U1. TinySwitch-II keeps on switching as long as the pull down current < 250  $\mu$ A. U1 will stop switching if the pull down current exceeds 250  $\mu$ A.

### 4.3 Output Rectification

When U1 Mosfet is turned ON, current flows through transformer primary and stores energy. When U1 is ON, output diode D20 is OFF. When the U1 Mosfet is OFF, D20 is forward biased, and the stored energy is transferred to the secondary and stores in C22, C23 and C25. The snubber C21 and R20 across secondary winding will improve EMI.

### 4.4 Output Feedback

Resistors R30, R31 divide down the supply output voltage and apply it to the reference pin of error amplifier U22. Shunt regulator U22 drives optocoupler U20 through resistor R28 to provide feedback information to the U1 EN pin. Capacitor C27 drives the optocoupler during supply startup to reduce output voltage overshoot. C26 plays a role in compensating of the power supply feedback loop.



#### **4.5 OTP, OVP and LPS Protection Circuit**

Q1, Q3, R11 and R21 form a SCR to pull BP pin act as a latch circuit. R8 is a thermal resistor of a NTC type. R8 and R9 form an OTP's trigger circuit of the SCR. The SCR will be triggered when temperature raise to OTP setting point.

D21, R27, R44, U23 and R1 form an OVP trigger circuit of the SCR. When output voltage raise to let D21 conducted, it will trigger the SCR for protection.

R33, C36, D24 and R36 form a LPS trigger circuit of the SCR. R33 and C36 set at about 300ms delay time for peak 4A output current testing. (The peak current testing is 4A/200ms/ 1A/us and 0.25A/ 1800ms/ 1A/us, and then the output voltage can't be less than 3V.) If the output load is increased, the bias voltage will be increased too. When the bias voltage increased to LPS setting point, it will let D24 conducted to trigger the SCR for protection.



### 5 PCB Layout


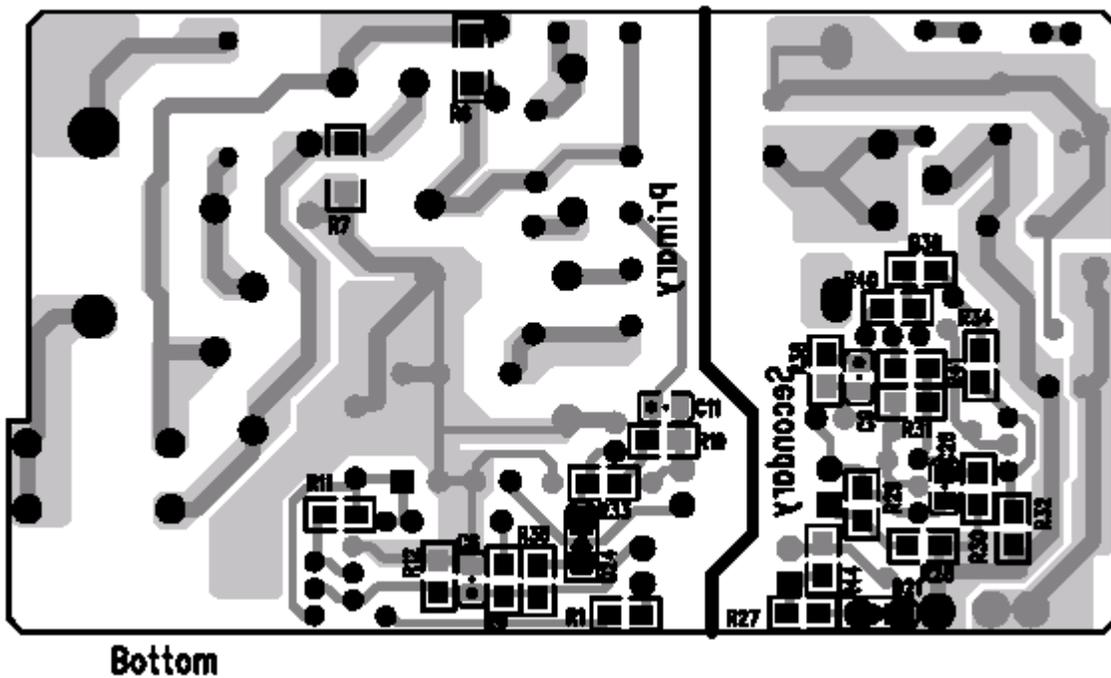


Figure 3 – Printed Circuit Layout

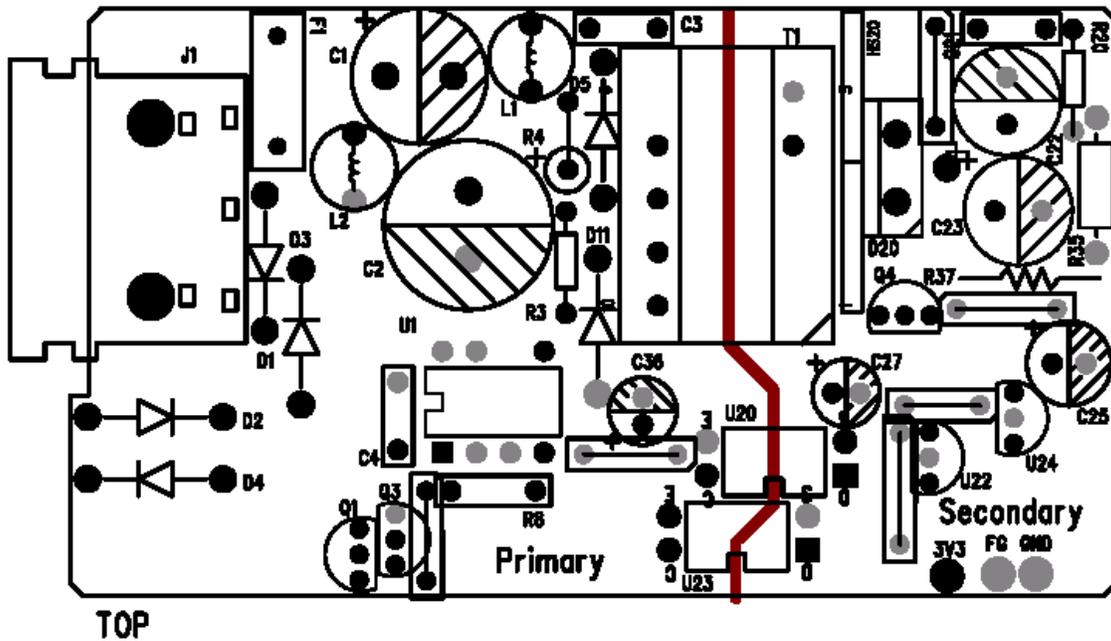

## 6 Bill Of Materials

Item	Quantity	Reference	Description	Part NO.
1	1	C1	10UF/400V	
2	1	C2	22UF/400V	
3	1	C3	2200pF/1KV	
4	4	C4,C8,C11,C26	100n	
5	1	C14	0.01U/250VAC	
6	1	C21	2.2nF/100V	
7	2	C22,C24	1000uF/6.3V	
8	1	C27	1U/16V	
9	1	C36	22U/50V	
10	5	D1,D2,D3,D4,D11	1A / 1000V	1N4007
11	1	D5	1A / 1000V	1N4007GP
12	1	D20	10A / 40V	MBR1040
13	1	D21	3V3/0.5W	
14	1	D24	30V/0.5W	
16	1	F1	FUSE 250V / 1A	
17	1	J1	AC INLET	AC INLET
18	1	L1	CHOKE 2mH	DR CORE
19	1	L2	CHOKE 1mH	DR CORE
20	1	Q1	PNP Transistor	2SA1015(PNP)
21	1	Q3	NPN Transistor	2SC1815(NPN)
22	3	R1,R27,R28	47R / 0805	
23	1	R3	200R / 0.5W	
24	1	R4	68K / 0.5W	
25	2	R6,R7	1K / 1206	
26	2	R8,R19	100K / 0805	
27	2	R9,R11	10K / 0805	
28	1	R12	2K7 / 0805	
29	1	R20	5R1/ 0.5W	
30	1	R29	1K / 0805	
31	1	R30	4K32,1%	
32	1	R31	10K,1%	
33	1	R33	4K7 / 0805	
34	1	R36	820R / 0805	
35	1	R44	470R / 0805	
36	1	T1	Transformer	EI22
37	1	U1	Tiny switch	TNY268P
38	2	U20,U23	Photo coupler	LTV817B
39	1	U22	TL431	



## 7 Transformer Specification

### 7.1 Electrical Diagram

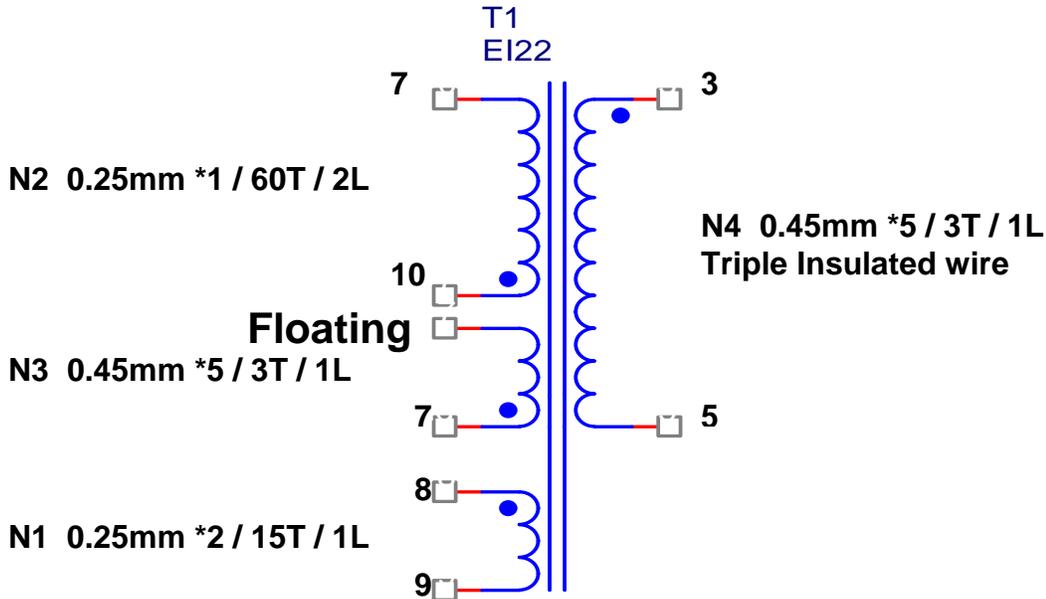


Figure 4 – Transformer Electrical Diagram

### 7.2 Electrical Specifications

<b>Electrical Strength</b>	1 second, 60 Hz, from Pins 1-5 to Pins 6-10	3000 VAC
<b>Primary Inductance</b>	Pins 7-10, all other windings open, measured at 100 kHz, 0.4 VRMS	1.18mH, +/-10%
<b>Resonant Frequency</b>	Pins 7-10, all other windings open	1MHz (Min.)
<b>Primary Leakage Inductance</b>	Pin 7-10 with Pin 3-5 shorted, measured at 100 kHz, 0.4 VRMS	30 $\mu$ H (Max.)

### 7.3 Materials

Item	Description
[1]	Core: PC40 EI22
[2]	Bobbin: EI 22, 10 Pin
[3]	Magnet Wire: 0.25mm heavy Nyleaze
[4]	Magnet Wire: 0.45mm heavy Nyleaze
[5]	Triple Insulated Wire: 0.55mm
[6]	Tape: 3M 1298 Polyester Film (yellow) 15mm, 0.26m Thick.
[7]	Tape: 3M 1298 Polyester Film (yellow) 10mm, 0.25mm Thick.
[8]	Varnish

**7.4 Transformer Build Diagram**

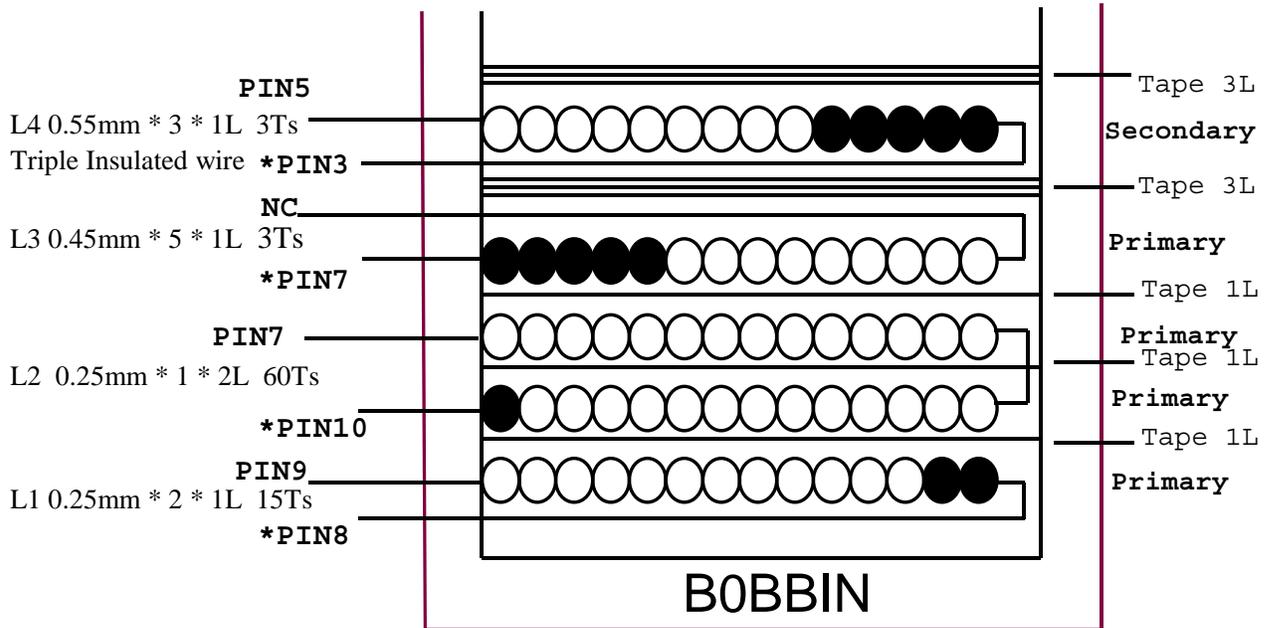


Figure 5 – Transformer Build Diagram

**7.5 Transformer Construction**

<b>Primary Layer</b>	Start at Pin 8. Wind 15 turns of item [3] from right to left. Finish at Pin 9.
<b>Insulation</b>	1Layer of tape [6] for insulation
<b>Primary Layer</b>	Start at Pin 10. Wind 60 turns / 2Layers of item [3]. Wind 1'st layer from left to right; and add 1 layer of tape [6] for insulation; and then wind 2'nd layer from right to left. Finish at Pin 7.
<b>Insulation</b>	1Layer of tape [6] for insulation
<b>Primary Layer</b>	Start at Pin 7. Wind 5-filar 3 turns of item [4] from right to left. Finish at NC.
<b>Insulation</b>	3Layers of tape [6] for insulation.
<b>Secondary Winding</b>	Start at Pin 3 Wind tri-filar 3 turns of item [5] from left to right. Finish at Pin 5.
<b>Insulation</b>	3Layers of tape [6] for insulation.
<b>Final Assembly</b>	Assemble and secure core halves. Put 3 Layers of item [7]. Impregnate uniformly with dip varnish [8]and bake.



## 8 Transformer Spreadsheets

### Power Supply Input

Var	Value	Output 1 (main)	Units	Description
VACMIN	85		Volts	Min Input AC Voltage
VACMAX	265		Volts	Max Input AC Voltage
FL	50		Hertz	Line Frequency
TC	2.51		mSeconds	Diode Conduction Time
Z	0.58			Loss Allocation Factor

### Power Supply Outputs

Var	Value	Output 1 (main)	Units	Description
VOx		3.50	Volts	Output Voltage
IOx		3.00	Amps	Output Current

### Device Variables

Var	Value	Output 1 (main)	Units	Description
Device	TNY268P			PI Device Name
PO	10.5		Watts	Total Output Power
VDRAIN	563		Volts	Maximum Drain Voltage
VDS	3.18		Volts	Drain to Source Voltage
FSNOM	132000		Hertz	TinySwitch-II Switching Frequency
FSMIN	120000		Hertz	Minimum Switching Frequency
FSMAX	144000		Hertz	Maximum Switching Frequency
KRPKDP	0.47			Continuous/Discontinuous Operating Ratio Warning! KRP/KDP is too low Tip: Increase size of TinySwitch-II device, increase efficiency (N), increase reflected output voltage (VOR), increase minimum input voltage (VACMIN) or consider device family with larger power capability.
ILIMITMIN	0.51		Amps	Current Limit Minimum
ILIMITMAX	0.59		Amps	Current Limit Maximum
IRMS	0.29		Amps	Primary RMS Current
DMAX	0.50			Maximum Duty Cycle

### Power Supply Components Selection

Var	Value	Output 1 (main)	Units	Description
CIN	33.0		uFarads	Input Capacitance
VMIN	85.0		Volts	Minimum DC Input Voltage
VMAX	374.8		Volts	Maximum DC Input Voltage
VCLO	200		Volts	Clamp Zener Voltage
PZ	2.0		Watts	Primary Zener Clamp Loss
RLS1	2.0		MOhms	Line sense resistor

### Power Supply Output Parameters



Var	Value	Output 1 (main)	Units	Description
VDx		0.50	Volts	Output Winding Diode Forward Voltage Drop
PIVSx		22	Volts	Output Rectifier Maximum Peak Inverse Voltage
ISPx		9.88	Amps	Peak Secondary Current
ISRMSx		5.44	Amps	Secondary RMS Current
IRIPPLEx		4.54	Amps	Output Capacitor RMS Ripple Current

### Transformer Construction Parameters

Var	Value	Output 1 (main)	Units	Description
Core/Bobbin	EI22			Core Type
Core Manuf.	Generic			Core Manufacturer
Bobbin Manuf	Generic			Bobbin Manufacturer
LPmin	1207		uHenries	Minimum Primary Inductance
NP	60.0			Primary Number of Turns
OD Actual	0.23		mm	Primary Actual Wire Diameter
Primary Current Density	7		A/mm <sup>2</sup>	Primary Winding Current Density
VOR	80.00		Volts	Reflected Output Voltage
BW	8.45		mm	Bobbin Winding Width
M	0.0		mm	Safety Margin Width
L	2.00			Primary Number of Layers
AE	42.00		mm <sup>2</sup>	Core Cross Sectional Area
ALG	335		nH/T <sup>2</sup>	Gapped Core Effective Inductance
BM	291		milliTesla	Maximum Flux Density
BAC	59		milliTesla	AC Flux Density for Core Loss
LG	0.14		mm	Gap Length
LL	24.1		uHenries	Primary Leakage Inductance
LSEC	20		nHenries	Secondary Trace Inductance

### Secondary Parameters

Var	Value	Output 1 (main)	Units	Description
NSx		3.0		Secondary Number of Turns
Rounded Down NSx				Rounded to Integer Secondary Number of Turns
Rounded Down Vox			Volts	Volts
Rounded Up NSx				Rounded to Next Integer Secondary Number of Turns
Rounded Up Vox			Volts	Auxiliary Output Voltage for Rounded up to Next Integer Secondary Number of Turns



---

ODS Actual Range		0.91 - 1.45	mm	Secondary Actual Wire Diameter Range Comment: Secondary wire size is greater than recommended maximum (0.4 mm) Tip: Consider a parallel winding technique (bifilar, trifilar) for >1.5 A outputs, increase size of transformer (larger BW), reduce margin (M).
------------------	--	----------------	----	--



## 9 Performance Data

All measurements performed at room temperature, 60 Hz input frequency.

### 9.1 Efficiency

9.1.1 Efficiency vs. input voltage at full load.

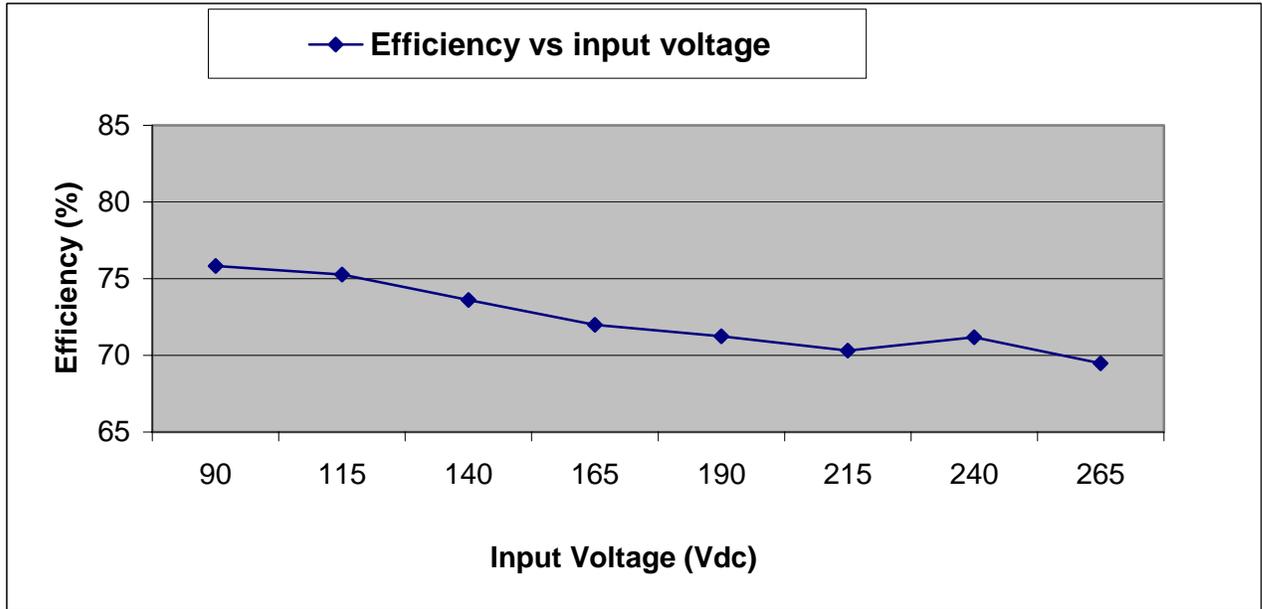


Figure 6 – Efficiency vs. Input Voltage, Room Temperature, 60 Hz.

9.1.2 Efficiency vs. output current at 115VAC / 230VAC

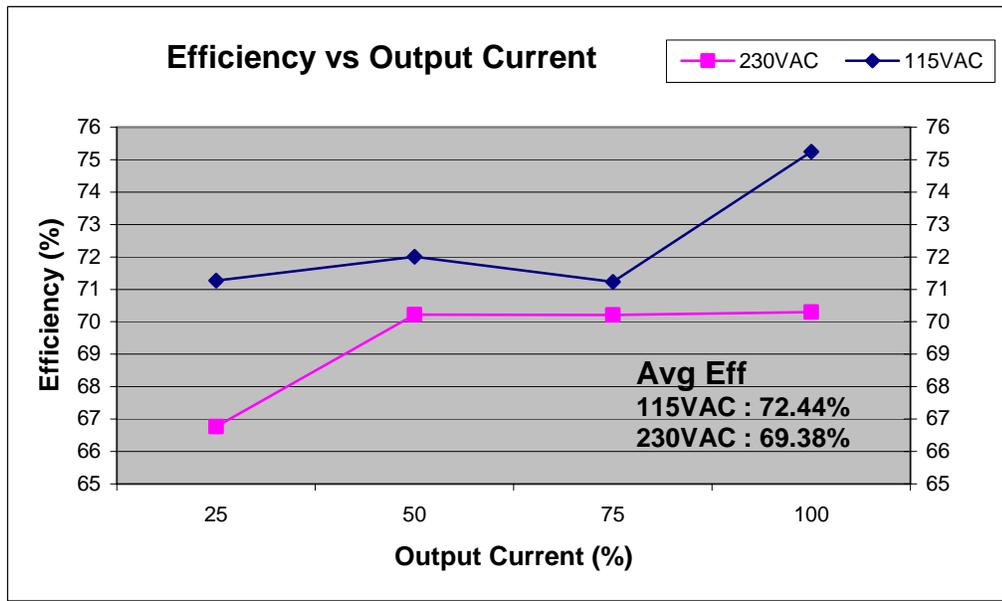


Figure 7 – Efficiency vs. Input Voltage, Room Temperature, 60 Hz.



### 9.2 No-load Input Power

#### 9.2.1 Input voltage vs. standby input power

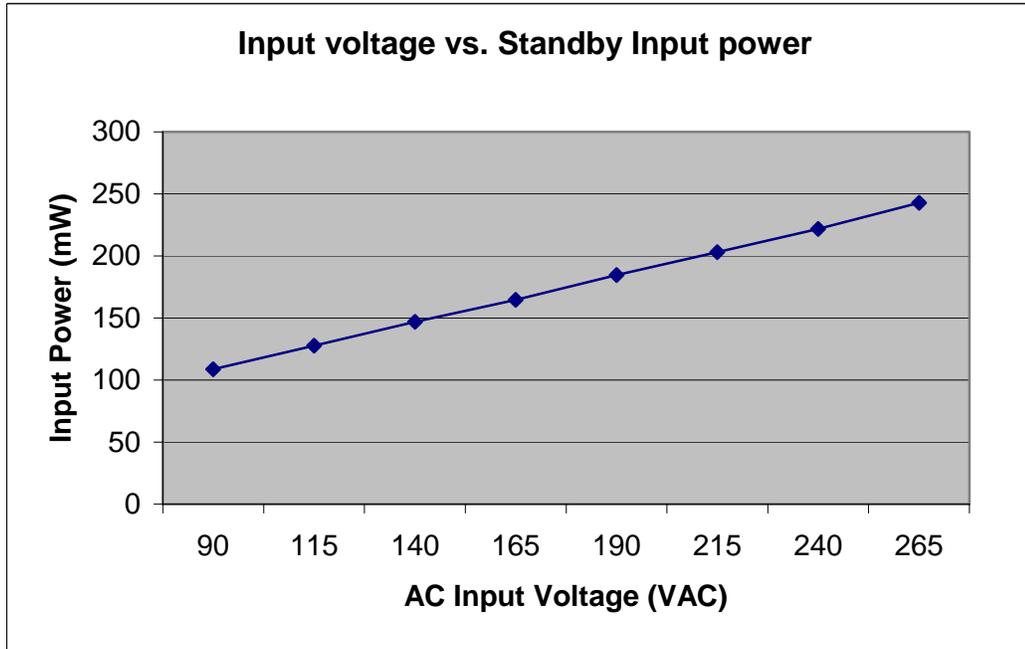


Figure 8 – Zero Load Input Power vs. Input Line Voltage, Room Temperature, 60 Hz.

#### 9.2.2 Input voltage vs. Input power (Po: 0.5W)

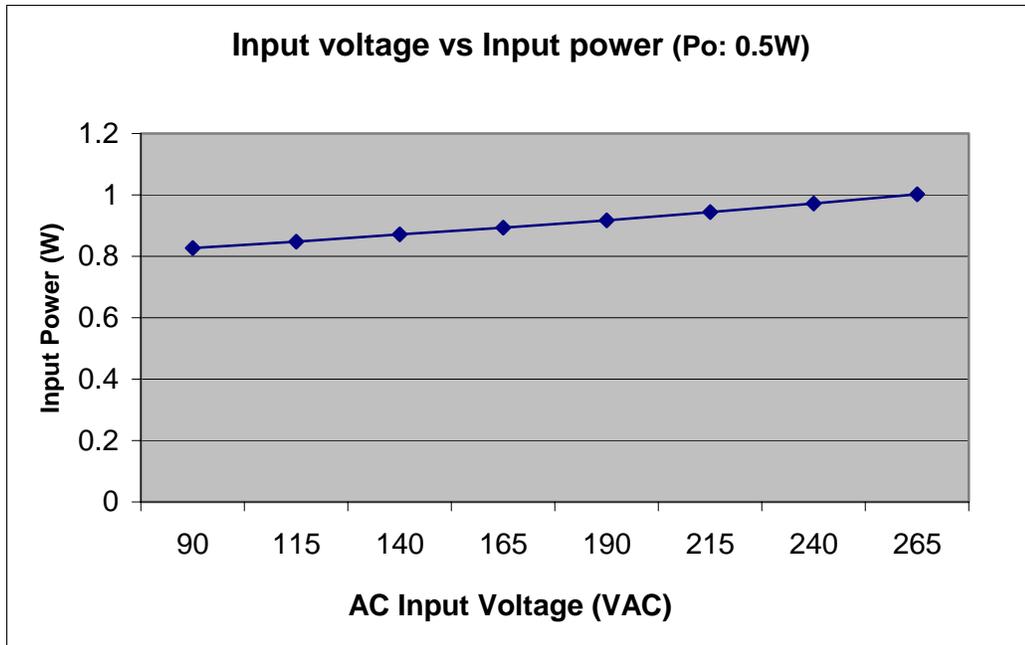


Figure 9 – Input Line Voltage vs. Input Power (Po: 0.5w), Room Temperature, 60 Hz.



### 9.3 Regulation

#### 9.3.1 Load

<b>Io (A)</b> <b>Vin (AC)</b>	<b>0</b>	<b>0.4</b>	<b>0.8</b>	<b>1.2</b>	<b>1.6</b>	<b>2</b>	<b>2.5</b>
<b>90V</b>	3.594	3.56	3.525	3.49	3.457	3.423	3.38
<b>265V</b>	3.594	3.56	3.527	3.49	3.457	3.422	3.38

Figure 10 – Load Regulation, Room Temperature

#### 9.3.2 Line

<b>Vin (ac)</b> <b>Vo (dc)</b>	<b>90</b>	<b>115</b>	<b>140</b>	<b>165</b>	<b>190</b>	<b>215</b>	<b>240</b>
<b>3.5V / 0A</b>	3.59	3.59	3.59	3.59	3.59	3.59	3.59
<b>3.5V / 2.5A</b>	3.37	3.37	3.37	3.37	3.37	3.37	3.37

Figure 11 – Line Regulation, Room Temperature, Full Load



## 10 Waveforms

### 10.1 Drain Voltage and Current, Normal Operation

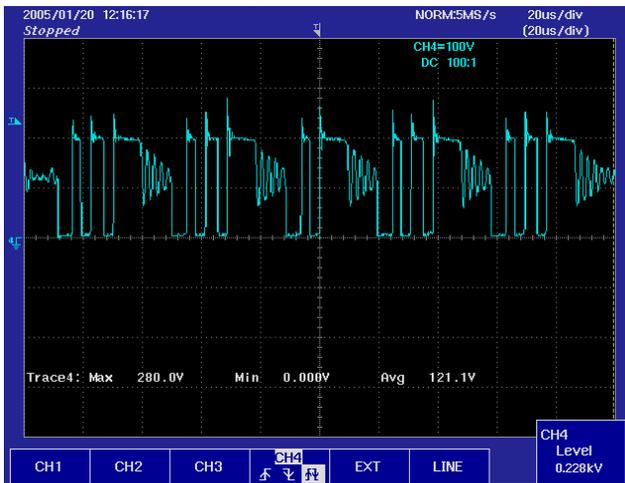


Figure 12– 90 VAC, Full Load.

Lower:  $V_{DRAIN}$ , 100 V / div, 20  $\mu$ s / div

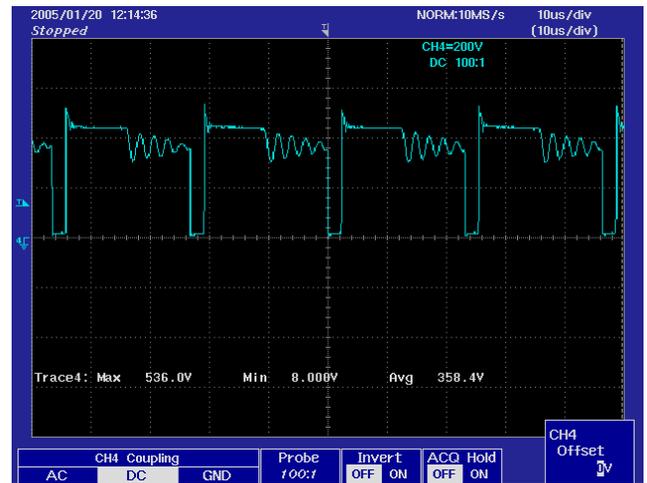


Figure 13 – 265 VAC, Full Load

Lower:  $V_{DRAIN}$ , 200 V / div, 10  $\mu$ s / div

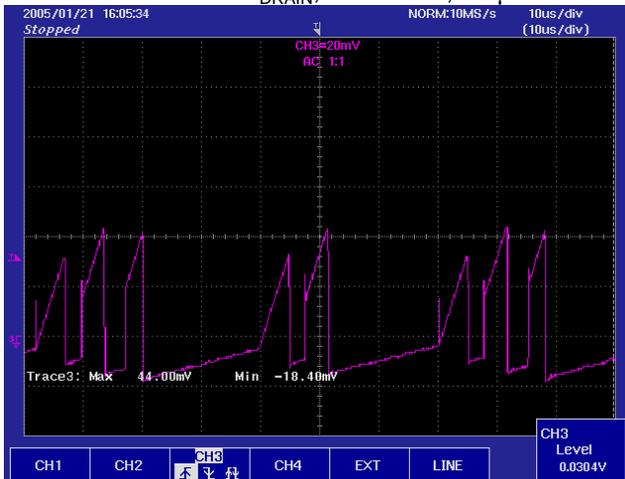


Figure 14 – 90 VAC, Full Load.

Lower:  $I_{DRAIN}$ , 200ma/ div, 10  $\mu$ s / div


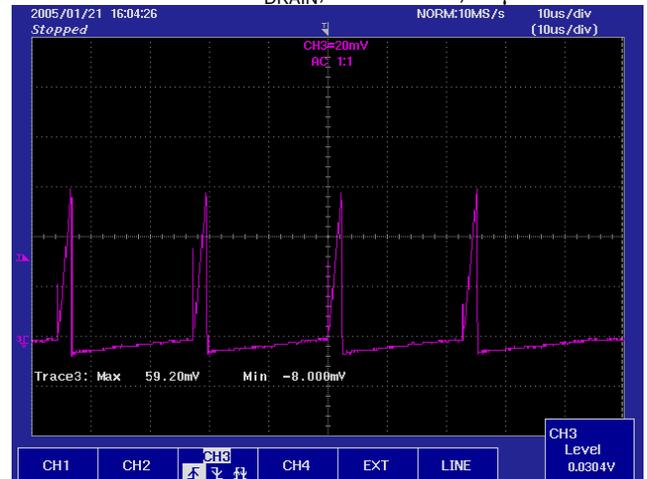


Figure 15 – 265 VAC, Full Load

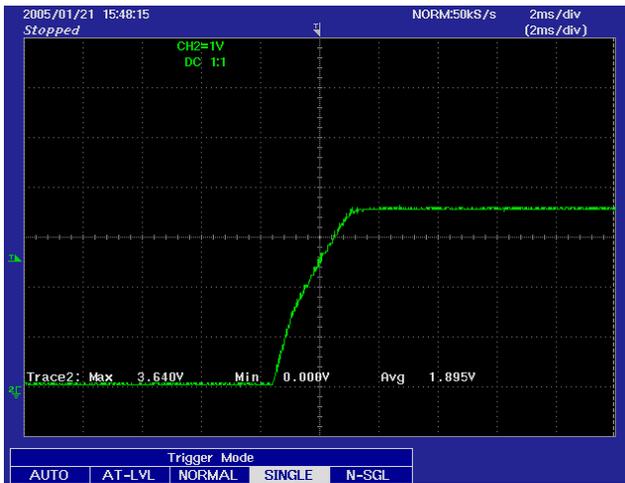
Lower:  $I_{DRAIN}$ , 200ma/ div, 10  $\mu$ s / div




### 10.2 Output Voltage Start-up Profile




**Figure 16** – Start-up Profile, 90VAC No Load  
1 V/ div, 2 ms / div.

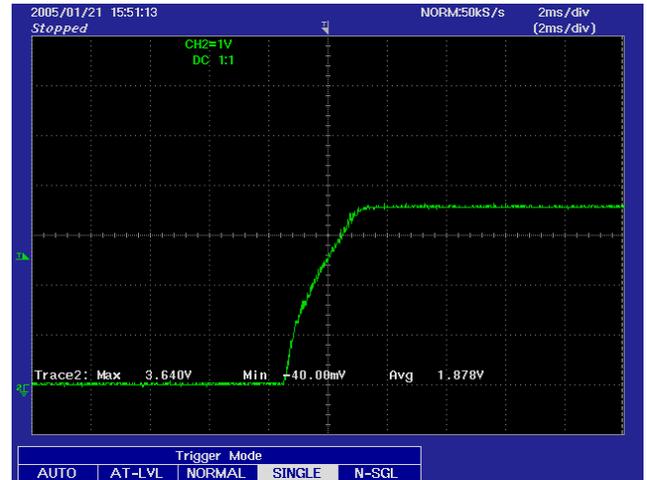

**Figure 17** – Start-up Profile, 265 VAC No Load  
1V/ div, 2 ms / div.

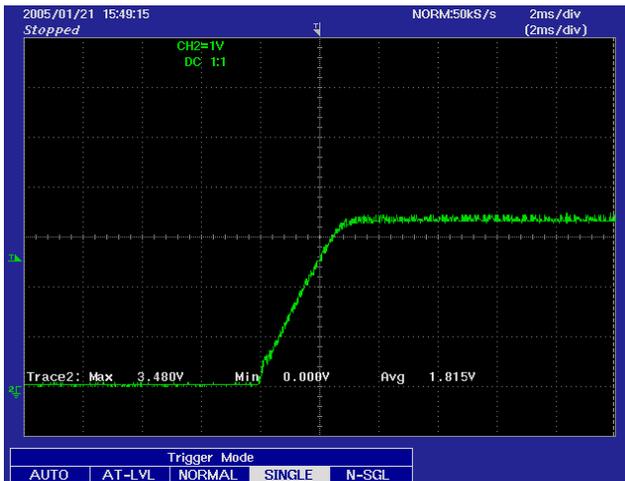

**Figure 18** – Start-up Profile, 90VAC Full Load  
1 V/ div, 2 ms / div.

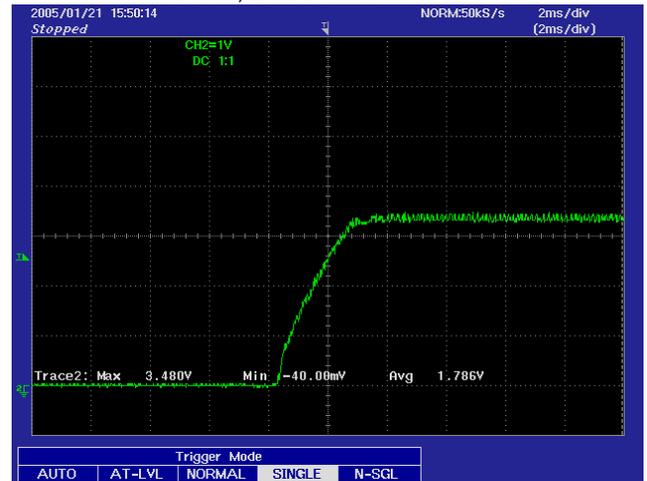

**Figure 19** – Start-up Profile, 265 VAC Full Load  
1V/ div, 2 ms / div.

### 10.3 Max Output Power (LPS) Testing (Specification $P_o < 17.5w$ )

Vin	$P_o < 17.5W$
90VAC	12.5W
264VAC	13.0W



### 10.4 Load Transient Response

Peak Load Transient Response, its Test Condition: 4A 200ms with 0.25A 2000ms, slew rate 1A/us

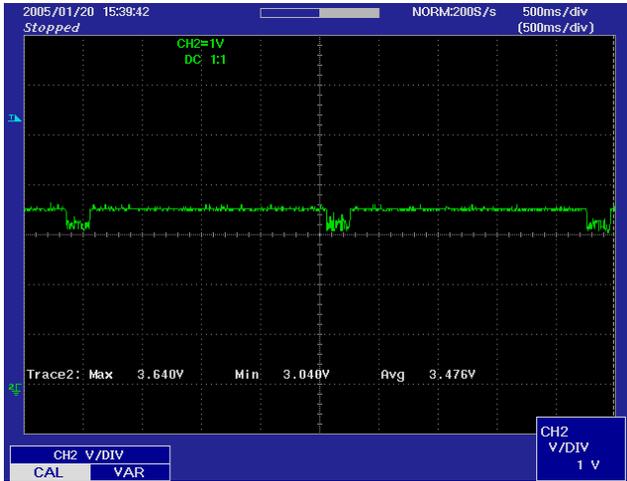


Figure 20 – 90 VAC, 3.5V output; 1V/ Div; 500ms/ Div.

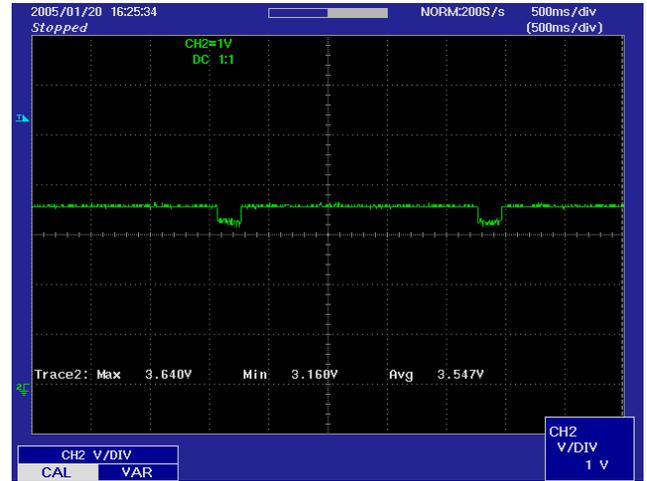


Figure 21 – 90 VAC, 3.5V output; 1V/ Div; 500ms/ Div.

Dynamic Load Response, its Test Condition: Test Condition: 2.5A 50ms with 0.25A 50ms, slew rate 1A/us

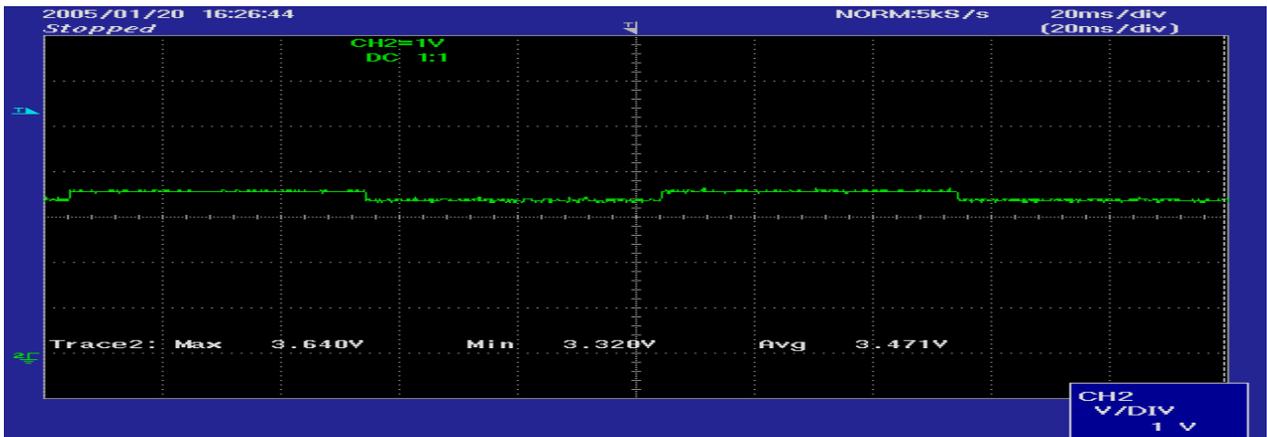


Figure 22 – 3.5V output; 1V/ Div; 20ms/ Div




## 10.5 Output Ripple Measurements

### 10.5.1 Ripple Measurement Technique

For DC output ripple measurements, a modified oscilloscope test probe must be utilized in order to reduce spurious signals due to pickup. Details of the probe modification are provided in Figure 23 and Figure 24.

The 5125BA probe adapter is affixed with two capacitors tied in parallel across the probe tip. The capacitors include one (1) 0.1  $\mu\text{F}/50\text{ V}$  ceramic type and one (1) 1.0  $\mu\text{F}/50\text{ V}$  aluminum electrolytic. **The aluminum electrolytic type capacitor is polarized, so proper polarity across DC outputs must be maintained (see below).**

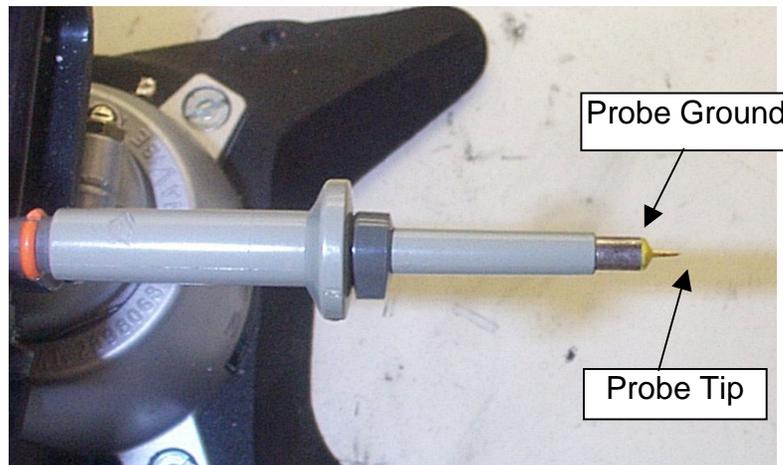

**Figure 23** – Oscilloscope Probe Prepared for Ripple Measurement. (End Cap and Ground Lead Removed)



**Figure 24** – Oscilloscope Probe with Probe Master 5125BA BNC Adapter. (Modified with wires for probe ground for ripple measurement, and two parallel decoupling capacitors added)

10.5.2 Measurement Results

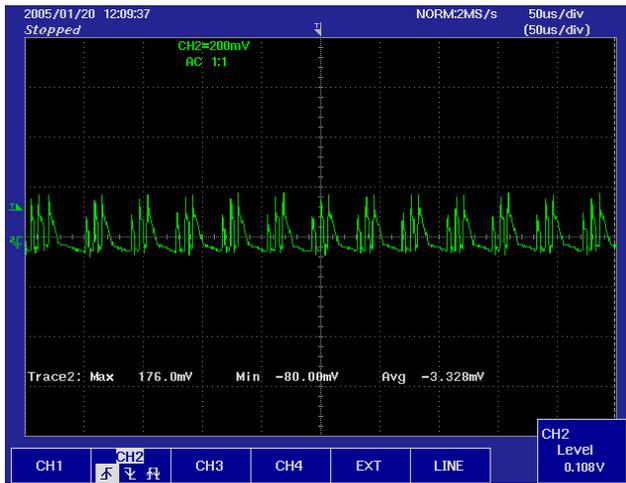


Figure 25 – 3.5V Ripple, 90 VAC, Full Load.  
50us/ div, 200 mV / div


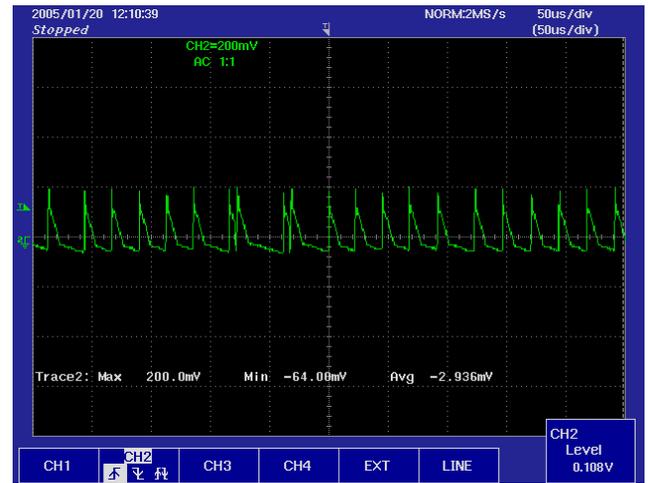


Figure 26 – 3.5V Ripple, 265 VAC, Full Load.  
50us/ div, 200 mV / div

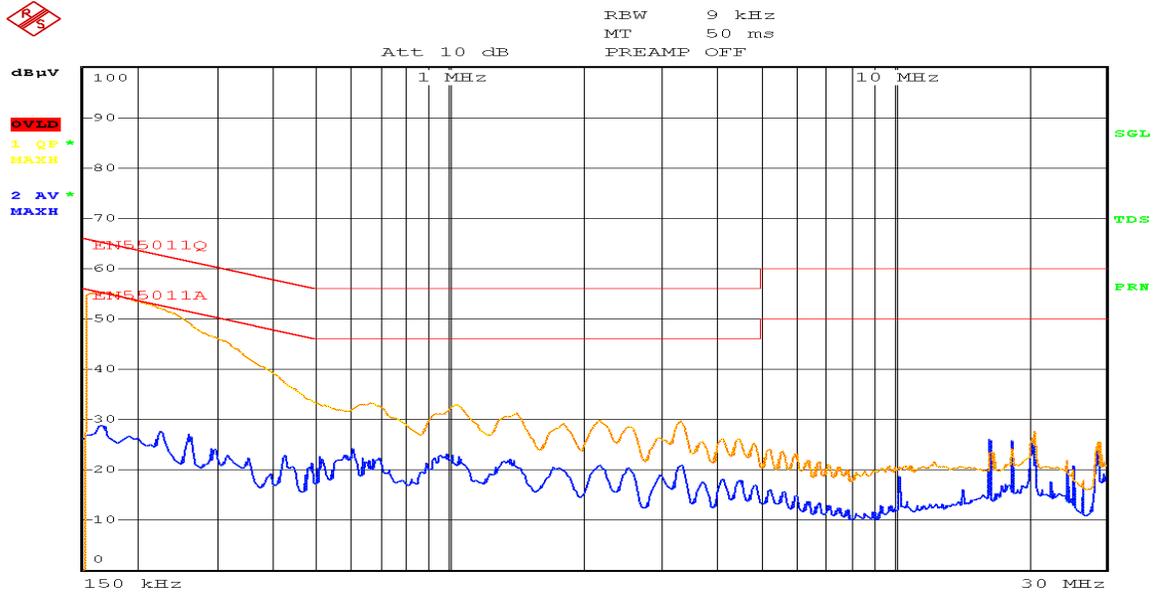


# 11 Conducted EMI



Comment B: A:\2MH BEAD.1A  
Date: 20.JAN.2005 09:28:25

Figure 27 – EMI Result: 115VAC, 60Hz, 3.5V 2.6A load, and EN55022 B Limits.

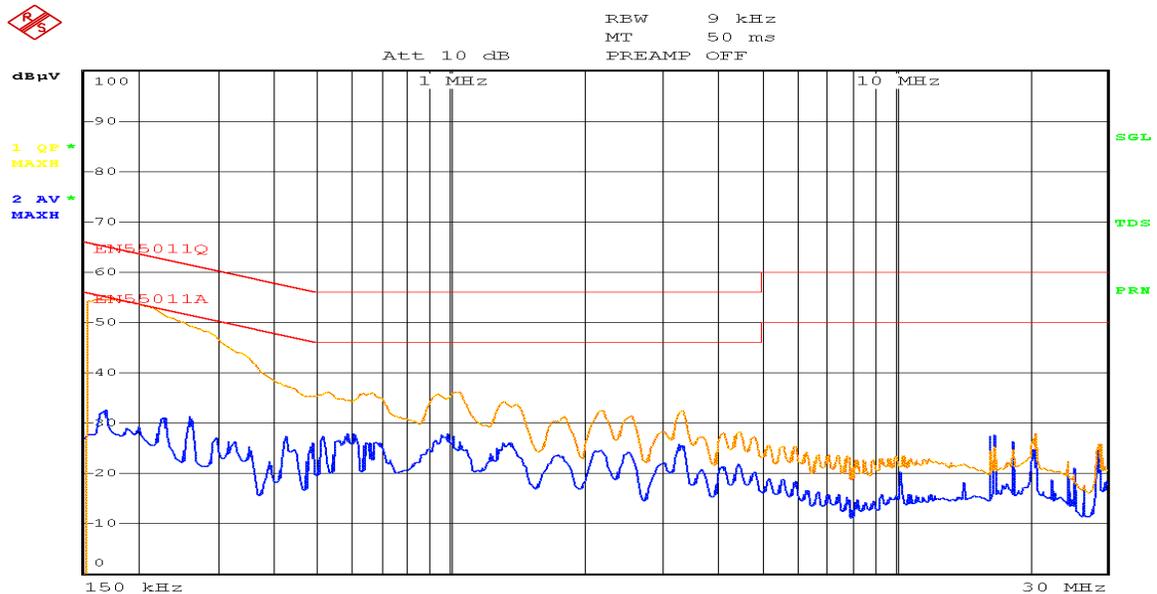

Comment B: A:\2MH BEAD.1A  
Date: 20.JAN.2005 09:20:51

Figure 28 – EMI Result: 230VAC, 60Hz, 3.5V 2.6A load, and EN55022 B Limits.



## 12 Revision History

<b>Date</b>	<b>Author</b>	<b>Revision</b>	<b>Description &amp; changes</b>	<b>Reviewed</b>
5-27-05	RS	1.0	Initial Release	KM / VC



For the latest updates, visit our Web site: [www.powerint.com](http://www.powerint.com)

Power Integrations may make changes to its products at any time. Power Integrations has no liability arising from your use of any information, device or circuit described herein nor does it convey any license under its patent rights or the rights of others. POWER INTEGRATIONS MAKES NO WARRANTIES HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS.

#### PATENT INFORMATION

The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at [www.powerint.com](http://www.powerint.com).

The PI Logo, **TOPSwitch**, **TinySwitch**, **LinkSwitch**, and **EcoSmart** are registered trademarks of Power Integrations. **PI Expert** and **DPA-Switch** are trademarks of Power Integrations.

© Copyright 2004, Power Integrations.

### Power Integrations Worldwide Sales Support Locations

#### WORLD HEADQUARTERS

5245 Hellyer Avenue,  
San Jose, CA 95138, USA  
Main: +1-408-414-9200  
Customer Service:  
Phone: +1-408-414-9665  
Fax: +1-408-414-9765  
e-mail:  
[usasales@powerint.com](mailto:usasales@powerint.com)

#### GERMANY

Rueckertstrasse 3,  
D-80336, Munich, Germany  
Phone: +49-895-527-3910  
Fax: +49-895-527-3920  
e-mail: [eurosales@powerint.com](mailto:eurosales@powerint.com)

#### JAPAN

Keihin-Tatemono 1st Bldg.  
12-20 Shin-Yokohama,  
2-Chome,  
Kohoku-ku, Yokohama-shi,  
Kanagawa 222-0033, Japan  
Phone: +81-45-471-1021  
Fax: +81-45-471-3717  
e-mail:  
[japansales@powerint.com](mailto:japansales@powerint.com)

#### TAIWAN

17F-3, No. 510,  
Chung Hsiao E. Rd., Sec. 5,  
Taipei, Taiwan 110, R.O.C.  
Phone: +886-2-2727-1221  
Fax: +886-2-2727-1223  
e-mail:  
[taiwansales@powerint.com](mailto:taiwansales@powerint.com)

#### CHINA (SHANGHAI)

Rm 807, Pacheer,  
Commercial Centre,  
555 Nanjing West Road,  
Shanghai, 200041, China  
Phone: +86-21-6215-5548  
Fax: +86-21-6215-2468  
e-mail:  
[chinasales@powerint.com](mailto:chinasales@powerint.com)

#### INDIA (TECHNICAL SUPPORT)

Innovatech  
261/A, Ground Floor  
7th Main, 17th Cross,  
Sadashivanagar  
Bangalore, India, 560080  
Phone: +91-80-5113-8020  
Fax: +91-80-5113-8023  
e-mail: [indiasales@powerint.com](mailto:indiasales@powerint.com)

#### KOREA

8th Floor, DongSung Bldg.  
17-8 Yoido-dong,  
Youngdeungpo-gu,  
Seoul, 150-874, Korea  
Phone: +82-2-782-2840  
Fax: +82-2-782-4427  
e-mail:  
[koreasales@powerint.com](mailto:koreasales@powerint.com)

#### UK (EUROPE & AFRICA HEADQUARTERS)

1st Floor, St. James's House  
East Street  
Farnham, Surrey GU9 7TJ  
United Kingdom  
Phone: +44-1252-730-140  
Fax: +44-1252-727-689  
e-mail: [eurosales@powerint.com](mailto:eurosales@powerint.com)

#### CHINA (SHENZHEN)

Rm# 1705, Bao Hua Bldg.  
1016 Hua Qiang Bei Lu,  
Shenzhen, Guangdong,  
518031, China  
Phone: +86-755-8367-5143  
Fax: +86-755-8377-9610  
e-mail:  
[chinasales@powerint.com](mailto:chinasales@powerint.com)

#### ITALY

Via Vittorio Veneto 12, Bresso,  
Milano,  
20091, Italy  
Phone: +39-028-928-6001  
Fax: +39-028-928-6009  
e-mail: [eurosales@powerint.com](mailto:eurosales@powerint.com)

#### SINGAPORE

51 Newton Road,  
#15-08/10 Goldhill Plaza,  
Singapore, 308900  
Phone: +65-6358-2160  
Fax: +65-6358-2015  
e-mail:  
[singaporesales@powerint.com](mailto:singaporesales@powerint.com)

#### APPLICATIONS HOTLINE

World Wide +1-408-414-9660

#### APPLICATIONS FAX

World Wide +1-408-414-9760

ER or EPR template – Rev 3.6 – Single sided

